

# ECE 105: Introduction to Electrical Engineering


Lecture 8

Circuit Problems - Recap

Yasser Khan

Rehan Kapadia


# Equivalent circuits

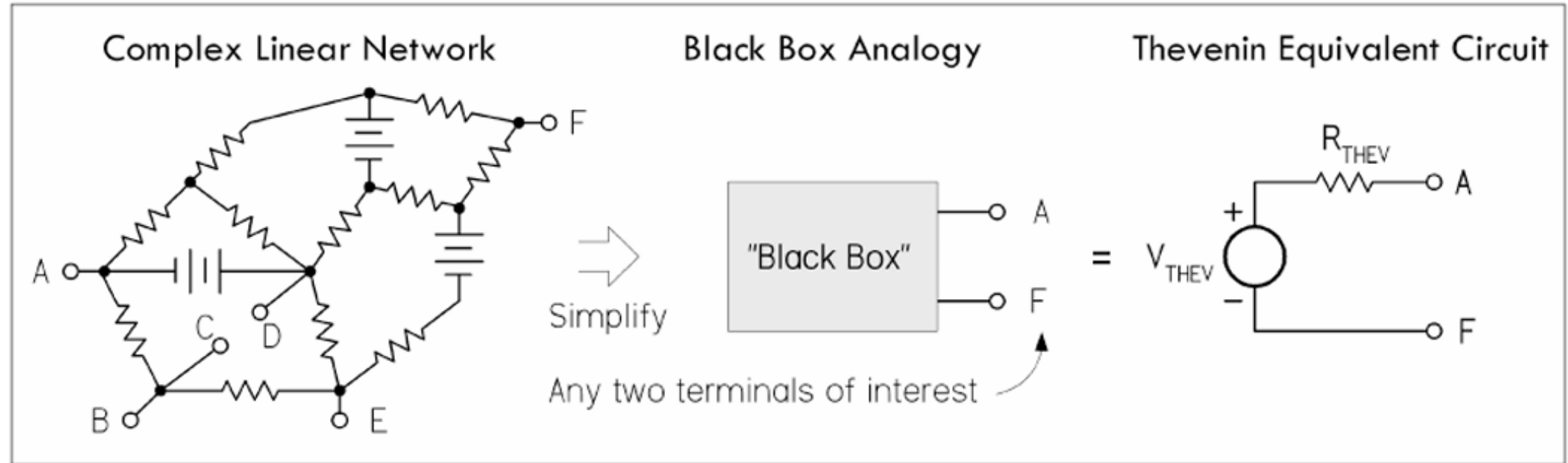


# Thevenin's equivalent circuit

## Thevenin's Theorem


### Real Circuit

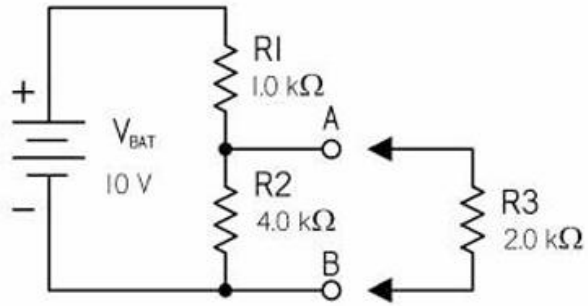


### Finding $V_{THEV}$

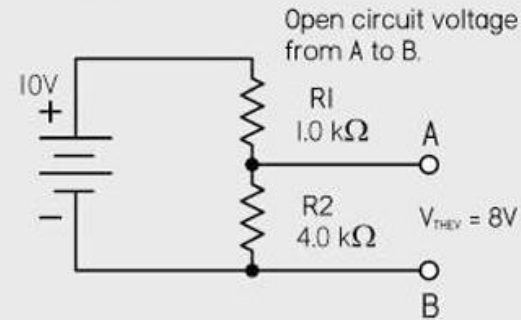

### Thevenin Equivalent Circuit

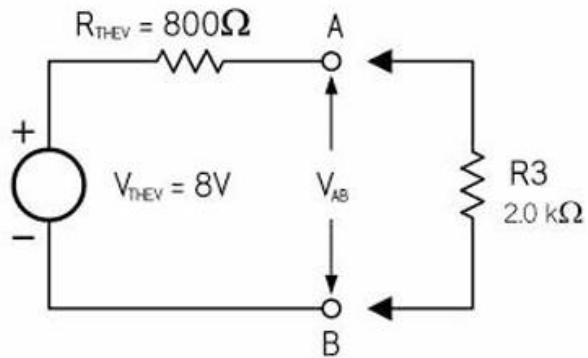


### Finding $R_{THEV}$

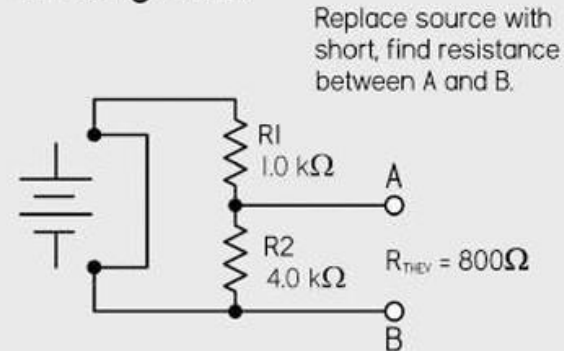


# Thevenin's equivalent circuit

## Thevenin's Theorem


### Real Circuit

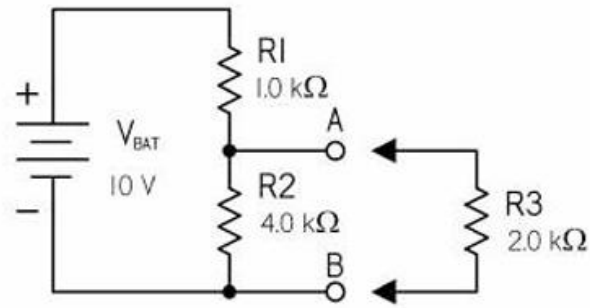




### Thevenin Equivalent Circuit

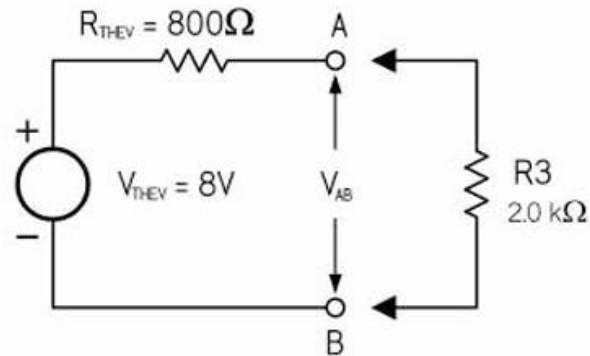

### Finding $V_{THEV}$

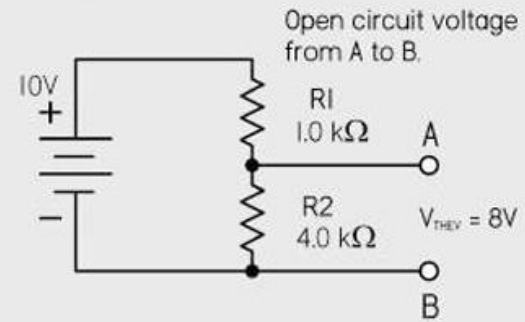


### Finding $R_{THEV}$

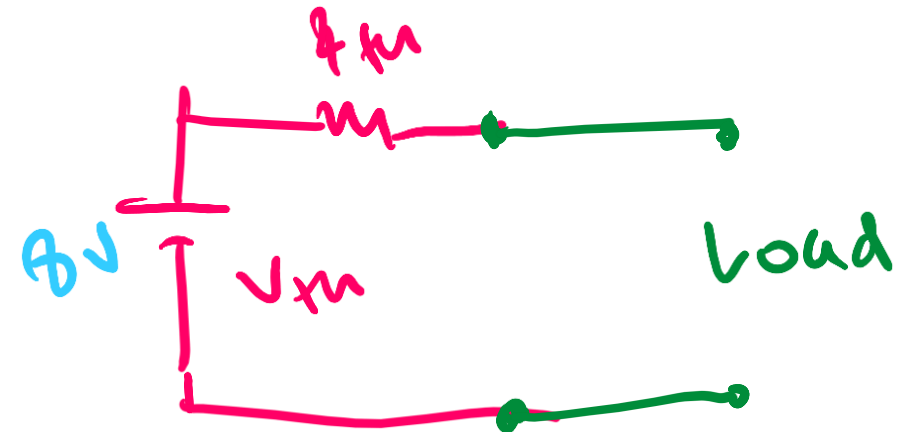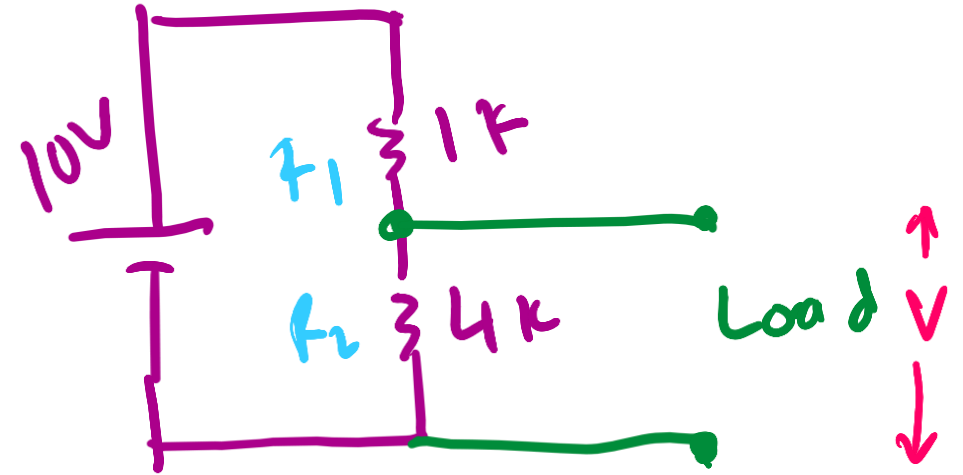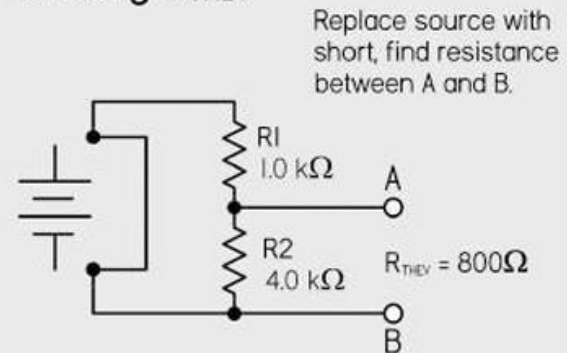


$$R_{THEV} = \frac{4 \cdot 10}{5} = 8V$$

# Thevenin's equivalent circuit

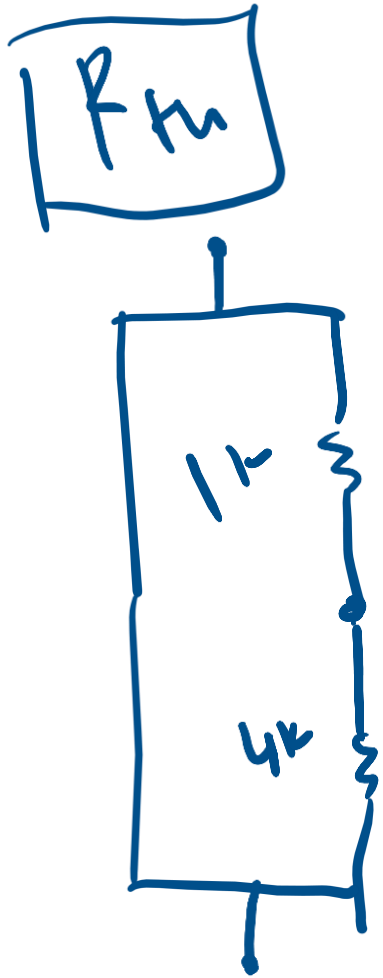


$$\frac{1}{R_{eq}} = \frac{1}{1k} + \frac{1}{4k}$$


$$= \frac{5}{1.4}$$

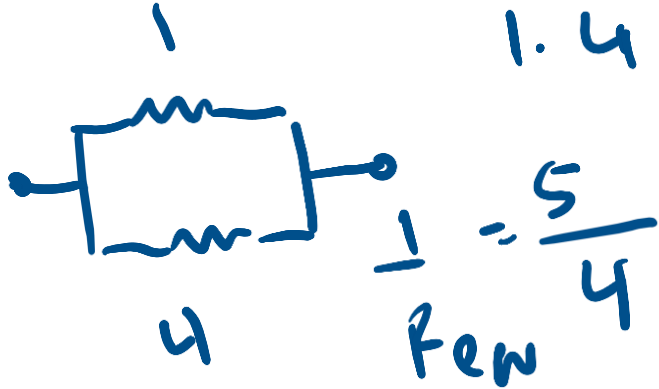

$$R_{eq} = 800 \Omega$$



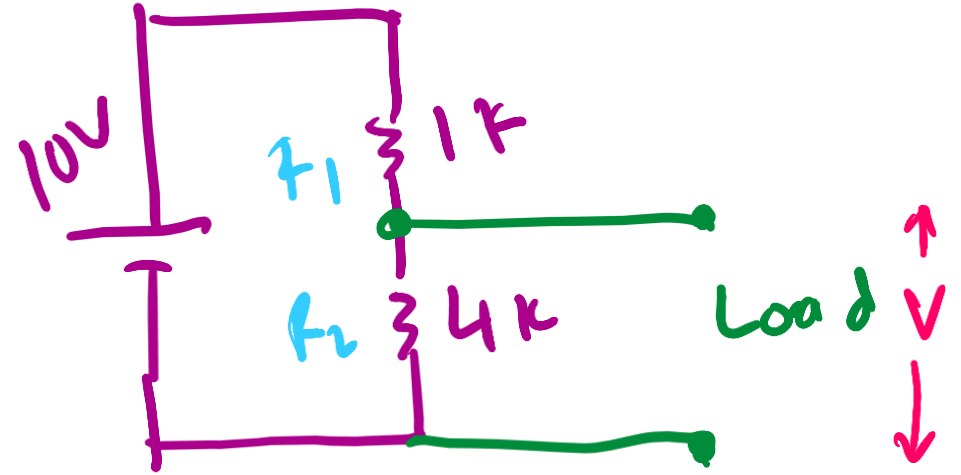


$$4k = 800 \Omega$$

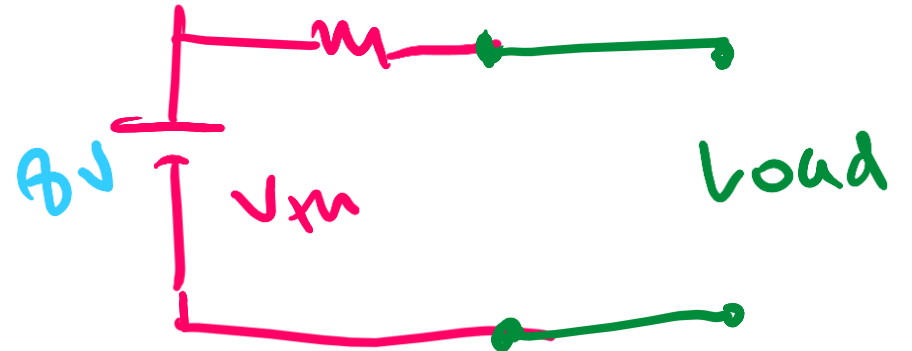


$$V_{th} = \frac{4 \cdot 10}{5} V = 8V$$

# Norton's equivalent circuit

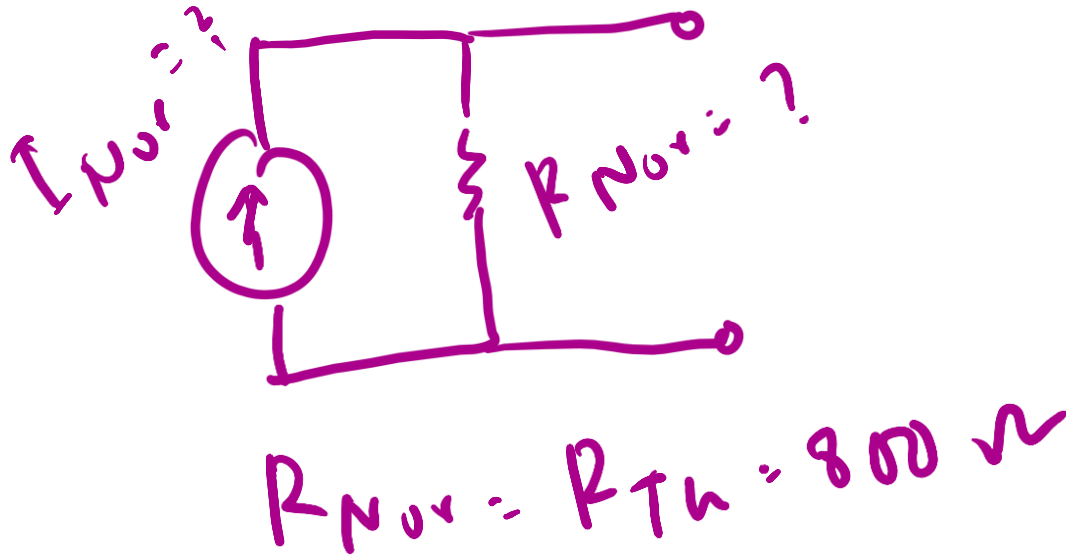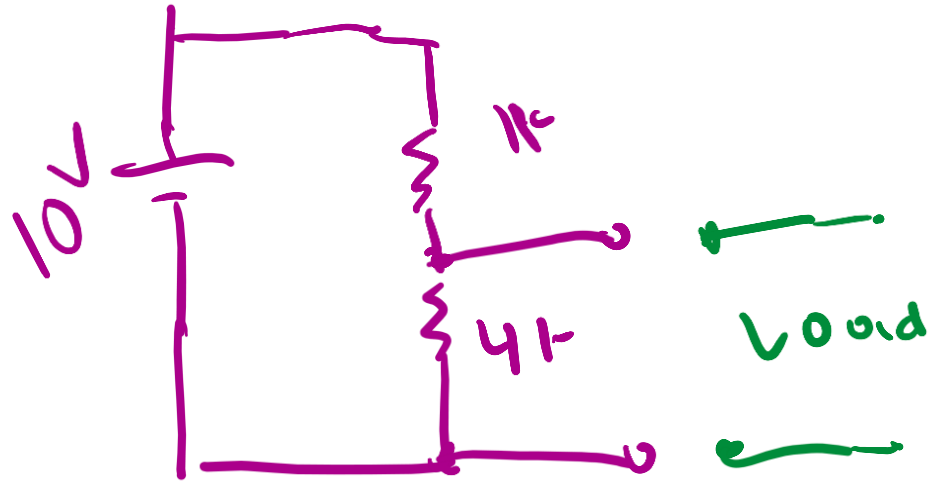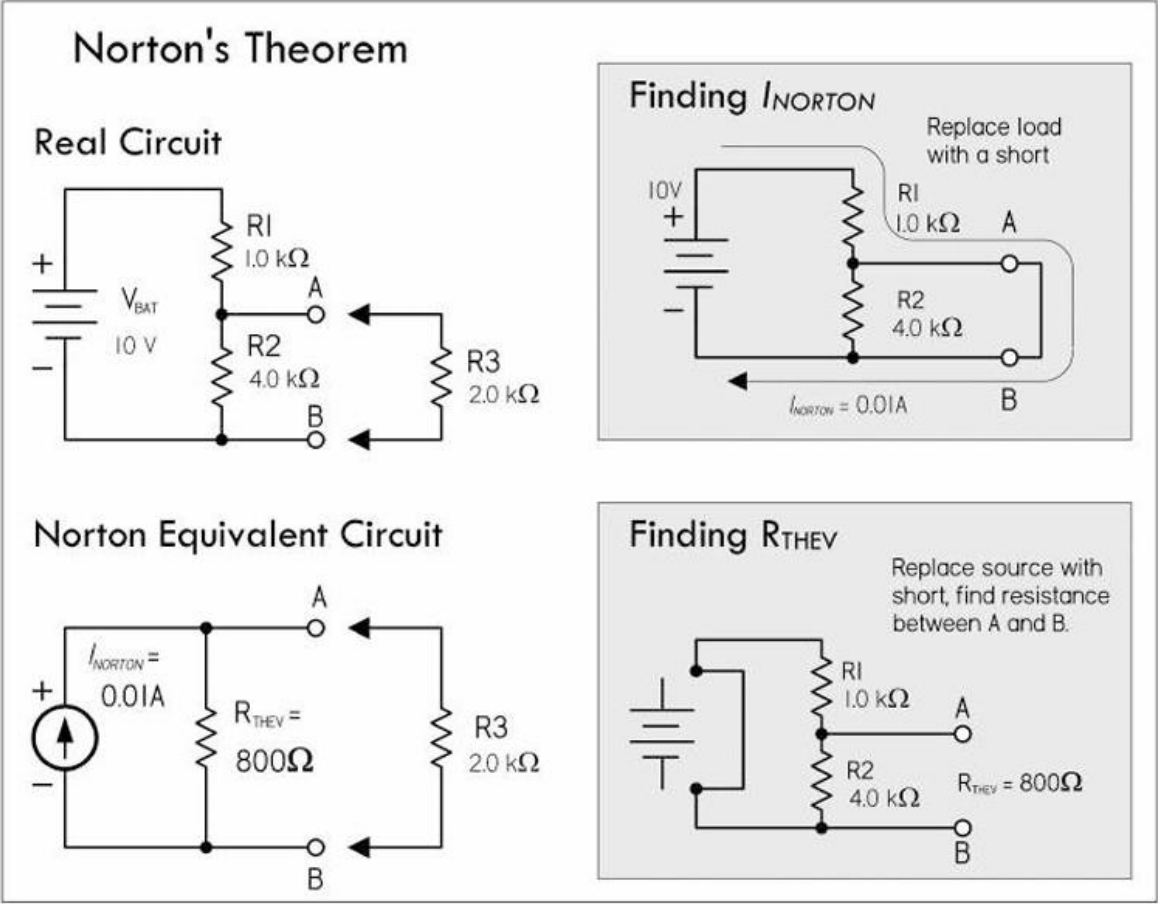

# Norton's equivalent circuit

Replace load with a  
Short.


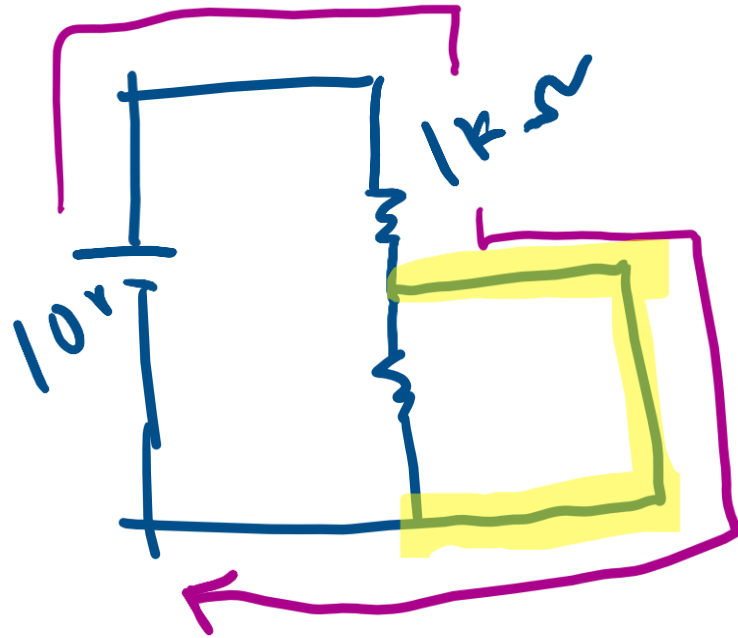


$$V = IR$$

$$I = \frac{V}{R} = \frac{10V}{1k}$$


$$= 0.01A$$

$$I_{NOR} = 0.01A$$

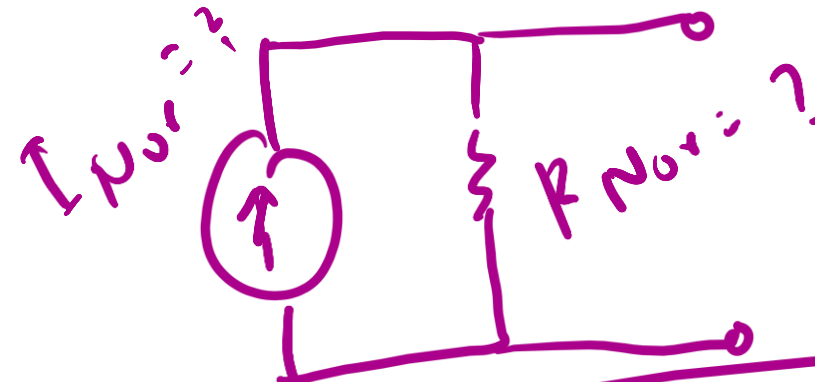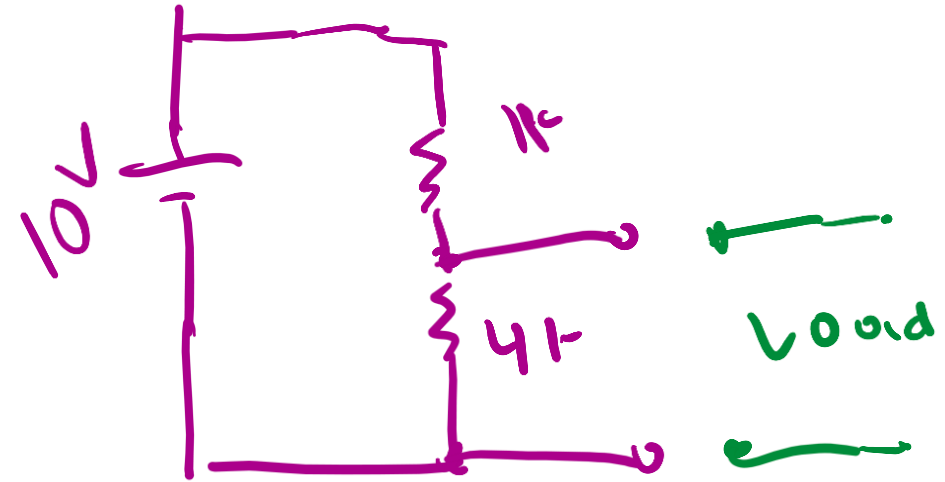


$$R_{NOR} = R_{TH} = 800\Omega$$


## Capacitor Symbols

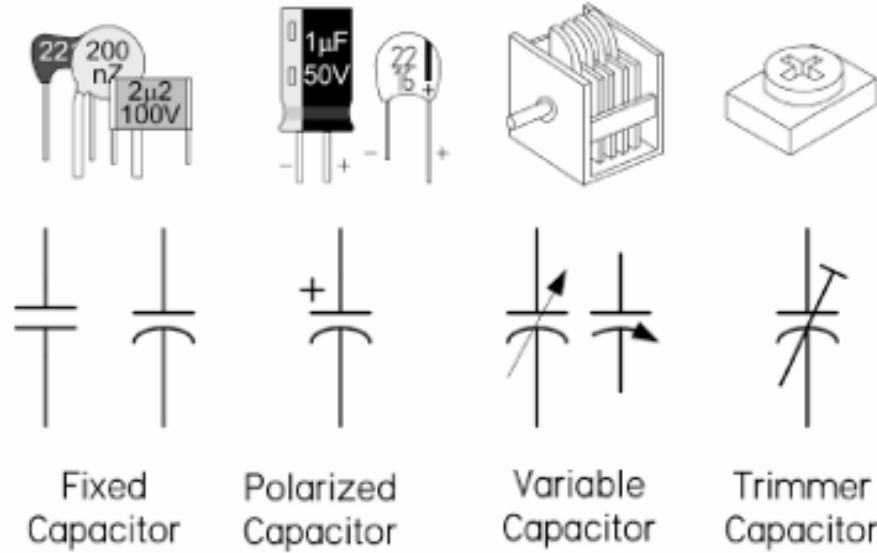

## Parallel Plate Capacitor

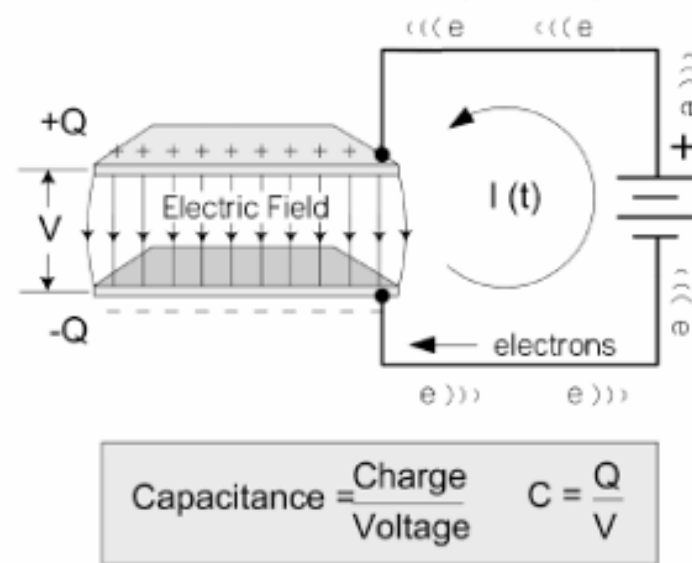


## Water Analogy

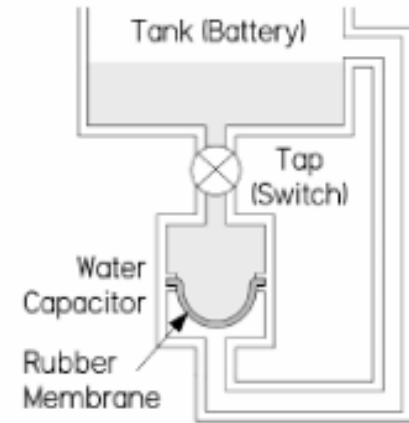



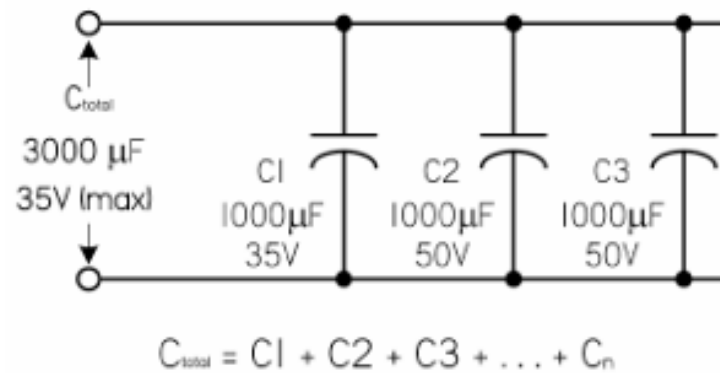
## Capacitors In Parallel

Increases the total capacitance, but limits max. voltage rating to that of smallest rated capacitor.



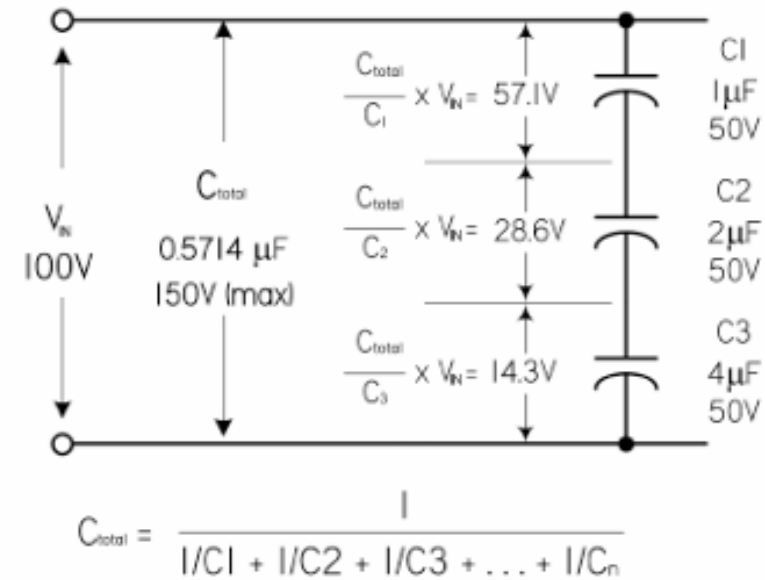
## Capacitors In Series

Increases max voltage rating, but decreases capacitance.




## Inductor Symbols


Air Core

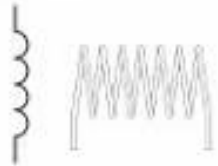


Adjustable

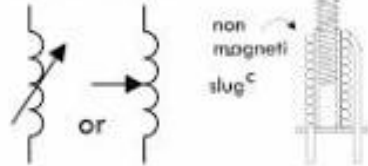


Magnetic or Iron Core

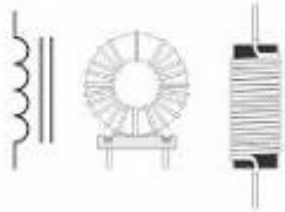


Ferrite Bead

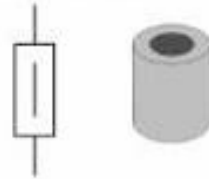


## Air-Core Inductor

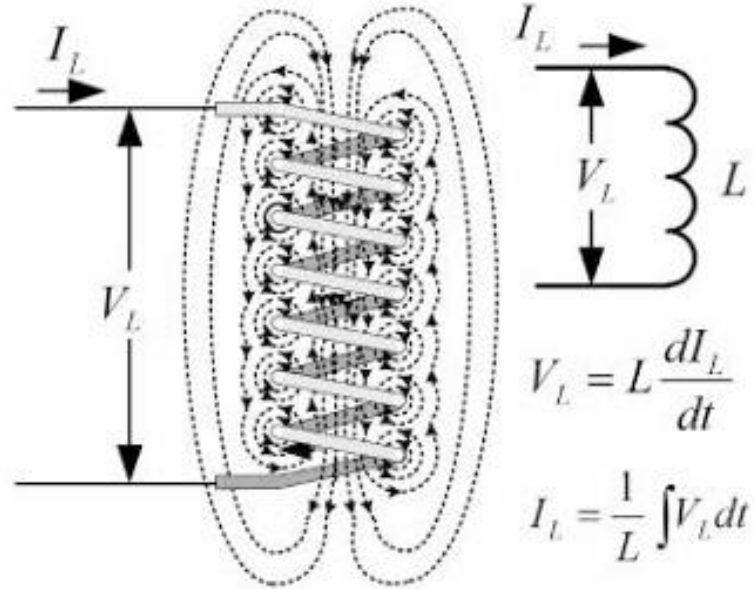


## Water Analogy

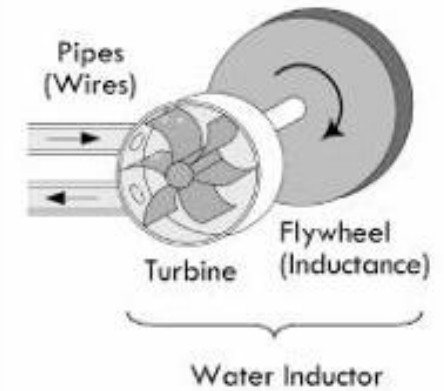

# Inductors

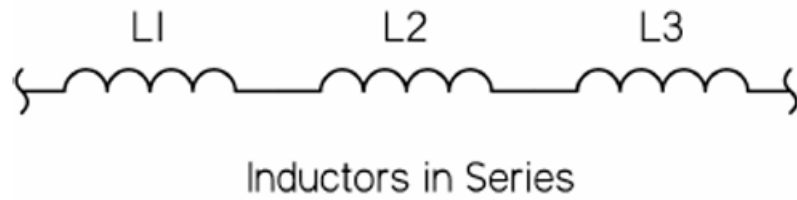


$$L_{\text{eq}} = L_1 + L_2 + L_3$$

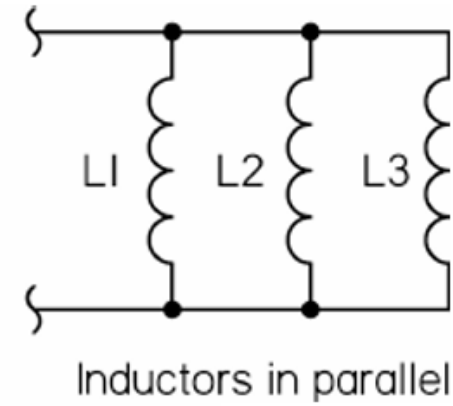

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$
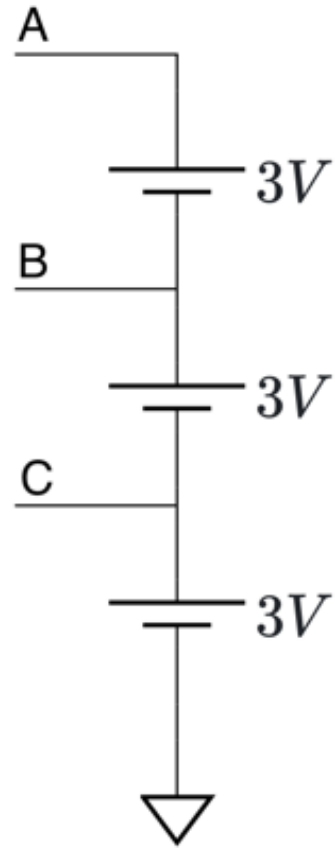
# Problem 1

Given the circuit diagram with nodes **A**, **B**, and **C**, each connected to **3V** sources as shown. Determine the voltages  $V_A$ ,  $V_B$ , and  $V_C$  at the respective nodes with respect to the ground.








# Voltage divider

# Current divider



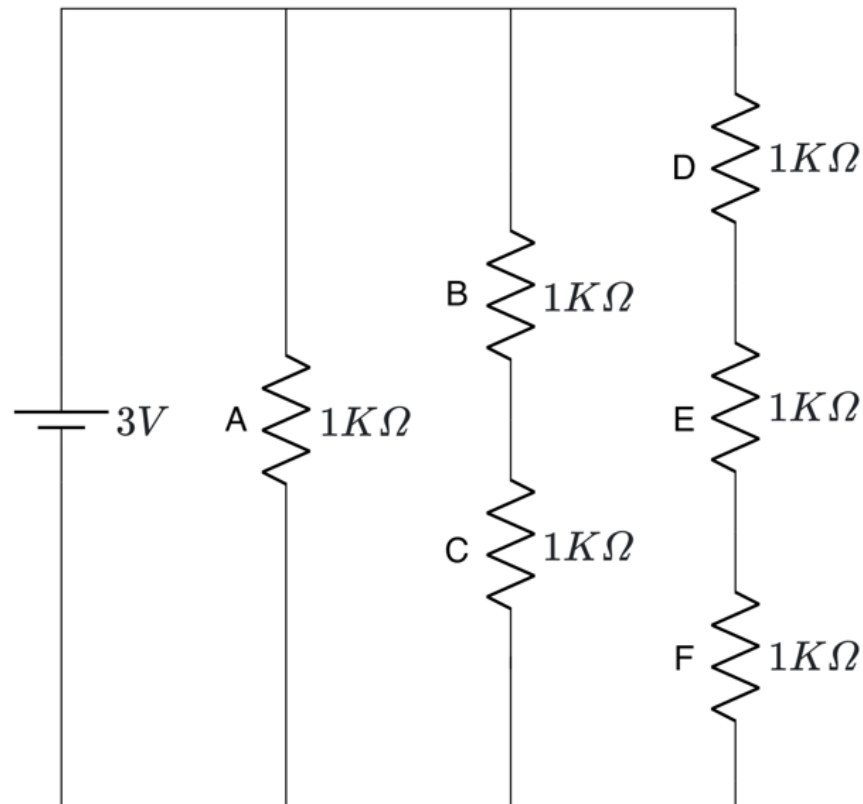
## Problem 2

Given the circuit with six resistors connected to a **3V** voltage source as shown. Find voltages across the resistors ( $V_A$ ,  $V_B$ ,  $V_C$ ,  $V_D$ ,  $V_E$ , and  $V_F$ ) and current through resistors ( $I_A$ ,  $I_B$ ,  $I_C$ ,  $I_D$ ,  $I_E$ , and  $I_F$ ).



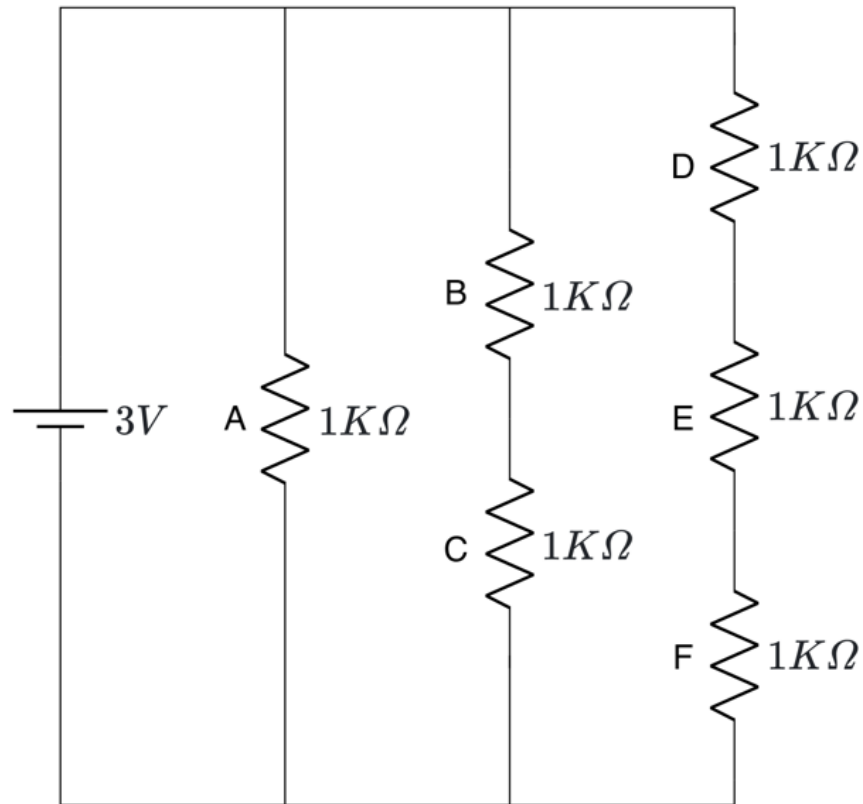
## Problem 2

Given the circuit with six resistors connected to a **3V** voltage source as shown. Find voltages across the resistors ( $V_A$ ,  $V_B$ ,  $V_C$ ,  $V_D$ ,  $V_E$ , and  $V_F$ ) and current through resistors ( $I_A$ ,  $I_B$ ,  $I_C$ ,  $I_D$ ,  $I_E$ , and  $I_F$ ).


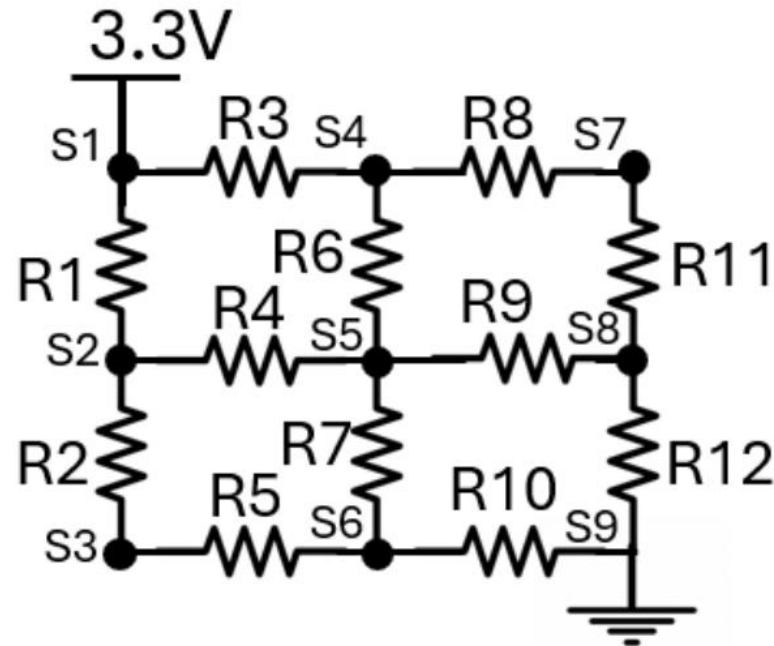
## Problem 3

Given the circuit diagram with nodes  $S_1$  to  $S_9$ ,  $S_1$  is connected to **3.3V** and GND (0V). Determine the voltages  $S_1$  to  $S_9$  at the respective nodes with respect to the ground if  $R_1$  to  $R_{12} = R$



## Problem 3

Given the circuit diagram with nodes  $S_1$  to  $S_9$ ,  $S_1$  is connected to **3.3V** and GND (0V). Determine the voltages  $S_1$  to  $S_9$  at the respective nodes with respect to the ground if  $R_1$  to  $R_{12} = R$

